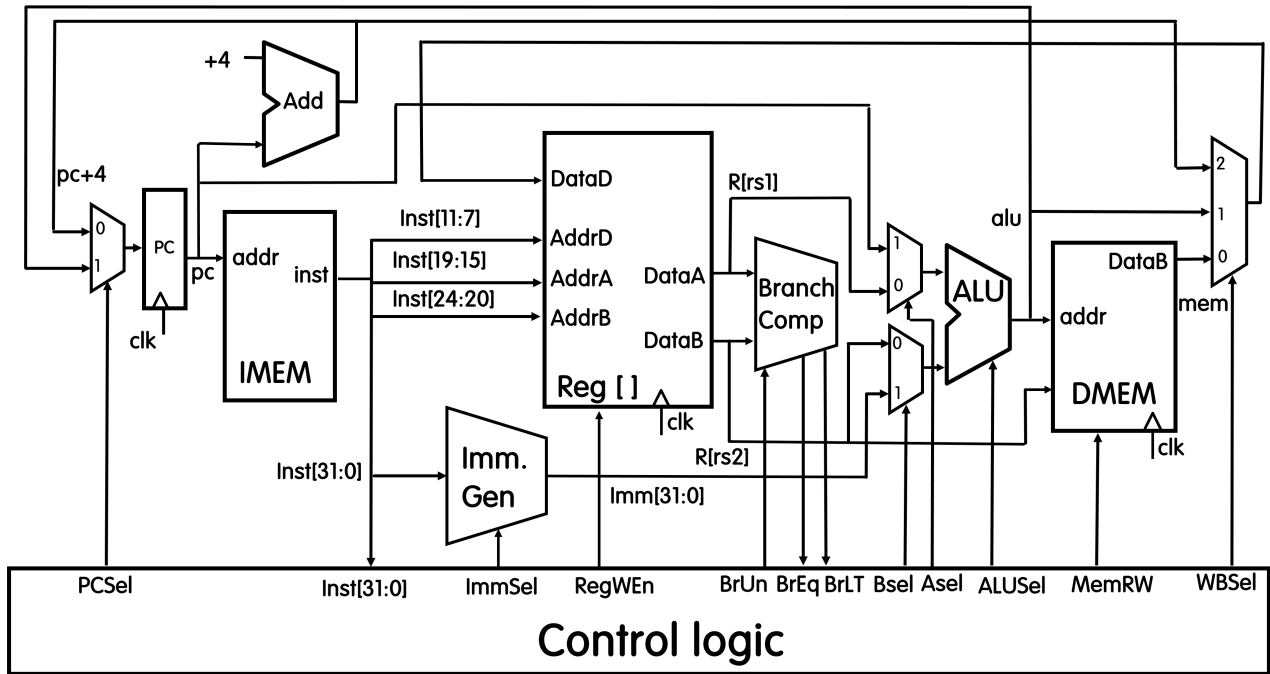


HW6.4. Datapath control signals

Consider the following datapath:



Suppose we have the following options for the ALUSel and ImmSel:

ALUSel	ALU operation	ImmSel	Immediate format
000	ADD: Result = A + B	00	I-type
001	SUB: Result = A - B	01	S-type
010	AND: Result = A & B	10	B-type
011	OR: Result = A   B	11	J-type
100	XOR: Result = A ^ B		
101	SLL: Result = A << B		
110	SRL: Result = A >> B		
111	Pass B: Result = B		

Now we are tasked to write the control signals for different instructions.

For each instruction listed below, write the corresponding control signals as a group of 13-bit binary code that follows the bit order below:

PCSel	RegWEn	ImmSel	BrUn	ASEL	BSEL	ALUSel	MemRW	WBSel
1 bit	1 bit	2 bits	1 bit	1 bit	1 bit	3 bits	1 bit	2 bits

For control signals that are not relevant to the instruction, put "X" for every bit of the control signal

As an example, the **addi** instruction will have the following control signals:

PCSel	RegWEn	ImmSel	BrUn	ASEL	BSEL	ALUSel	MemRW	WBSel
0	1	00	X	0	1	000	0	01

Here's the explanation for the **addi** control signals:

**PCSel = 0**, because you just execute the next instruction after **addi** if ever (it's not a jump or branch instruction), so you just select pc+4 branch. PC+4 branch corresponds to multiplexer input 0.

**RegWEn = 1**, because we have to write back to the register file to save the result of the **addi** instruction to rd.

**ImmSel = 00**, because **addi** is an I-type instruction, so you take in the I-type immediate. This corresponds to 00 according to the provided table.

**BrUn = X**, we technically don't care about this signal because we are not executing a branch instruction, so we put "X".

**ASEL = 0**, because we have to select the output from the register file (this is rs1). Register file output (rs1) corresponds to the multiplexer input 0.

**BSEL = 1**, because we have to select the immediate for the **addi** instruction. Immediate generator output corresponds to the multiplexer input 1.

Homework 6

Assessment overview

Total points: 0/100  
Score: 0%

Question

Value: 20

History:

Awarded points: 0/20

Report an error in this question

Previous question

Next question

Attached files

No attached files

Attach a file

Attach text

**ALUSel = 000**, because we have to select the addition operation on the ALU. This corresponds to 000 according to the provided table.

**MemRW = 0**, because we don't have to write to the memory.

**WBSel = 01**, because we have to select the output of the ALU to be written back to the register file. ALU output corresponds to the multiplexer input 1 (so binary 01).

This 13-bit code can then be written as **0100X01000001**

Now it's your turn. For the following instructions, write the corresponding 13-bit binary string (without the 0b prefix) that would correspond to the control signals to properly execute the instruction. **All answers should be 13 bits long.**

**or** instruction

?

**lw** instruction

?

**sw** instruction

?

**jal** instruction

?

**bgeu** instruction (*assume that the branch condition is true in this case*)

?

Save & Grade 20 attempts left

Save only

Additional attempts available with new variants ?